



Course Name: Embedded Systems

Course Number and Section: 14:332:368:01

Lab: [Lab # [2] – The only time you have to do math]

Professor: Phil Southard

Date Submitted: 03/07/2019

Submitted by: [Timothy Langer RUID# 189005424]

PRE-LAB

Single Bit Full Adder Truth Table

| Cin | B | A | Y | cout |
|-----|---|---|---|------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Write the logic equations for a single bit full adder with inputs A, B, Cin, and outputs Y, Cout.

Y:

Handwritten derivation of the logic equation for the sum output Y of a single-bit full adder:

$$Y = \overline{C_{in}}\overline{B}A + \overline{C_{in}}B\overline{A} + C_{in}\overline{B}\overline{A} + C_{in}BA$$
$$Y = \overline{C_{in}}(B \oplus A) + C_{in}(A \oplus B)$$


$\downarrow \quad \quad \downarrow$
 $x \quad \quad \overline{x}$

$$Y = \overline{C_{in}}x + C_{in}\overline{x}$$
$$Y = C_{in} \oplus x$$
$$Y = C_{in} \oplus A \oplus B$$


Cout :

$$\begin{aligned}C_{out} &= \bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in} \\C_{out} &= C_{in}[\bar{A}B + A\bar{B}] + [C_{in} + \bar{C}_{in}]AB \\C_{out} &= C_{in}[A \oplus B] + AB\end{aligned}$$

 Single Bit Adder(ADDER) Black Box Diagram:



ripple_adder Box Diagram:

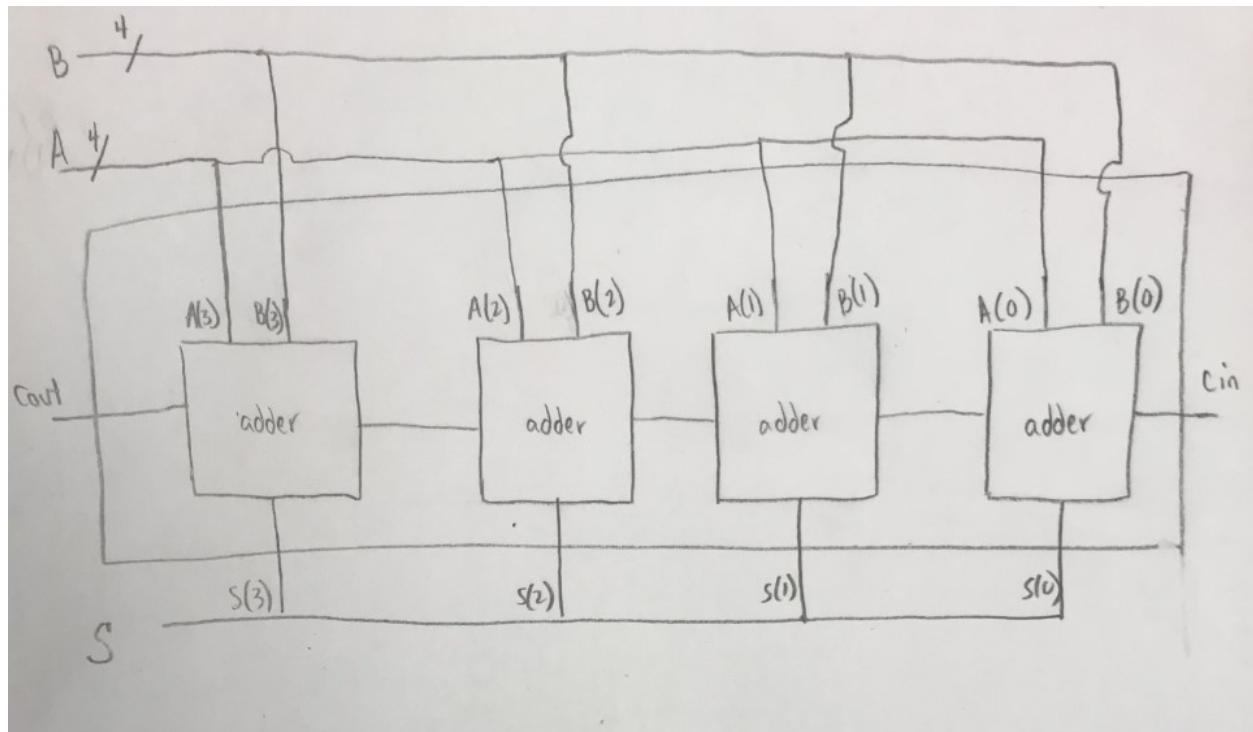

PURPOSE:

The purpose of this lab is to be able to understand and create a multi-bit adder and how a multi-function ALU is created in vhdl and implemented in a circuit. Part 1 helped to understand how from scratch, a single bit adder is created and is used to create a 4 bit adder. Starting with truth tables, they are used to create boolean expressions that represent the outputs such as Y, and Cout. Using a Karnaugh map, the logic can be minimized and a gate level description can be made to represent the data flow. This lab also helps to further understand structural design methodology by incorporating multiple single bit adders to create a 4-bit adder.

The purpose of part 2 of this lab is to understand the power of VHDL's numeric_std library. The important aspect is that this library contains many of the basic arithmetic and logical functions. They are already defined and synthesizable without having to create your own VHDL code. Therefore a multi-function ALU can be made without having to spend the time creating a hardware implementation for each function.

PART 1

Theory of Operation:


This part begins with the construction of a single-bit full adder called **adder**. From the logic created from the truth table, which also matches the gate level schematic provided in the lab instructions, the single bit adder was made. Then by connecting four of them together in the top design called **ripple_adder**, this made a 4-bit adder. This **ripple_adder** has an input of **Cin**, 4-bit input **A**, and 4-bit input **B**. With an output **Cout**, and 4-bit output **S**.

This circuit can be used under a few scenarios. First we can use it to add two 4-bit numbers. To do so, the **Cin** on the ripple counter should be set to zero. This circuit should then be able to correctly add two 4-bit numbers. If the answer resulted in an overflow, the overflow bit will set the **Cout** bit high, or a '1'. If there is no overflow, then the circuit will run as intended.


Another situation this **ripple_adder** can be used for, can be chains of **ripple_adders**. To connect them together the **Cin** of a ripple adder would connect to the **Cout** of another ripple adder. Together they can now represent an 8-bit adder. This 8-bit adder will also have a **Cin** input and a **Cout** output. Meaning the chain can be made even longer. The adder can be 4Bit, 8bit, 12bit and so on.

A test bench was then used to simulate the circuit. It successfully simulated the circuit as expected.

Single bit-adder “adder” SCHEMATIC:

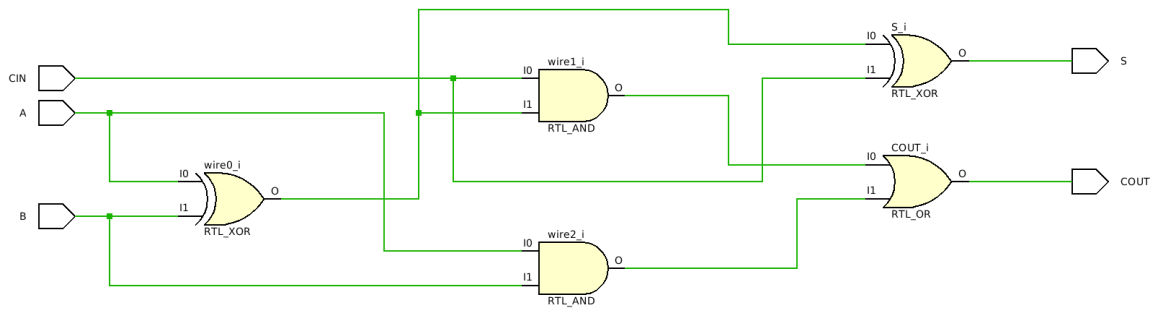

4-bit adder, “ripple_adder” SCHEMATIC:

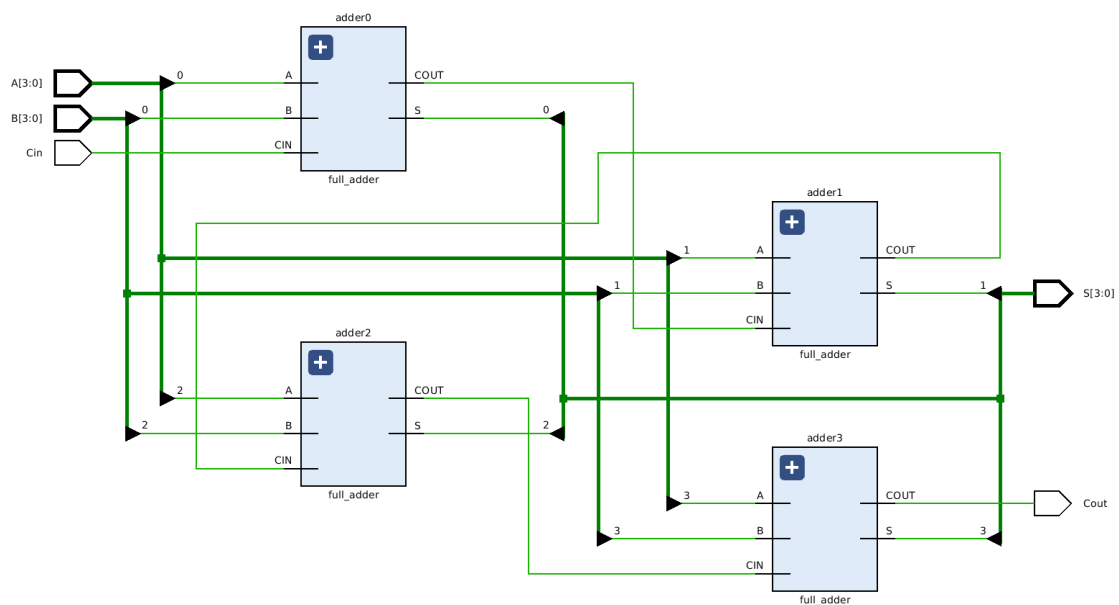

VHDL CODE:

single bit adder “adder”:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity full_adder is
    Port ( B : in STD_LOGIC;
          A : in STD_LOGIC;
          CIN : in STD_LOGIC;
          S : out STD_LOGIC;
          COUT : out STD_LOGIC);
end full_adder;

architecture Behavioral of full_adder is
    signal wire0, wire1, wire2 : std_logic;
begin

    wire0 <= a xor b;
    S<= wire0 xor CIN;
    wire1 <= cin and wire0;
    wire2 <= a and b;
    cout <= wire1 or wire2;

end Behavioral;
```

4-bit ripple adder “ripple_adder”:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ripple_adder is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          Cin : in STD_LOGIC;
          S : out STD_LOGIC_VECTOR (3 downto 0);
          Cout : out STD_LOGIC);
end ripple_adder;

architecture Behavioral of ripple_adder is

    component full_adder
    Port(
    B : in STD_LOGIC;
```

```

A : in STD_LOGIC;
CIN : in STD_LOGIC;
S : out STD_LOGIC;
COUT : out STD_LOGIC
);
end component;
signal wire : std_logic_vector(3 downto 0);
begin
wire(0)<=Cin;

adder0: full_adder
port map(
B => B(0),
A=> A(0),
CIN=> wire(0),
S=> s(0),
COUT => wire(1)
);
adder1: full_adder
port map(
B => B(1),
A=> A(1),
CIN=> wire(1),
S=> s(1),
COUT => wire(2)
);
adder2: full_adder
port map(
B => B(2),
A=> A(2),
CIN=> wire(2),
S=> s(2),
COUT => wire(3)
);
adder3: full_adder
port map(
B => B(3),
A=> A(3),
CIN=> wire(3),
S=> s(3),
COUT => cout
);

end Behavioral;

```


testbench code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ripple_counter_tb is
end ripple_counter_tb;

architecture Behavioral of ripple_adder_tb is

component ripple_adder is
Port
(A : in STD_LOGIC_VECTOR (3 downto 0);
 B : in STD_LOGIC_VECTOR (3 downto 0);
 Cin : in STD_LOGIC;
 S : out STD_LOGIC_VECTOR (3 downto 0);
 Cout : out STD_LOGIC);
end component;

signal A,B: std_logic_vector( 3 downto 0) := (others => '0');
signal S: std_logic_vector( 3 downto 0);
signal cin: std_logic := '0';
signal cout: std_logic;
begin

UUT: ripple_adder
Port map(
A => A,
B=> B,
cin => cin,
s=>S,
cout =>cout
);

stimulus : process
begin

cin <='0';
A <= "1111";
B <= "1111";
wait for 100 ns;
A <= "0000";
B <= "0000";
wait for 100 ns;

A<= "0110";
```

B<= "0110";


wait for 40 ns;

wait;


end process;

end Behavioral;

Simulation Window:

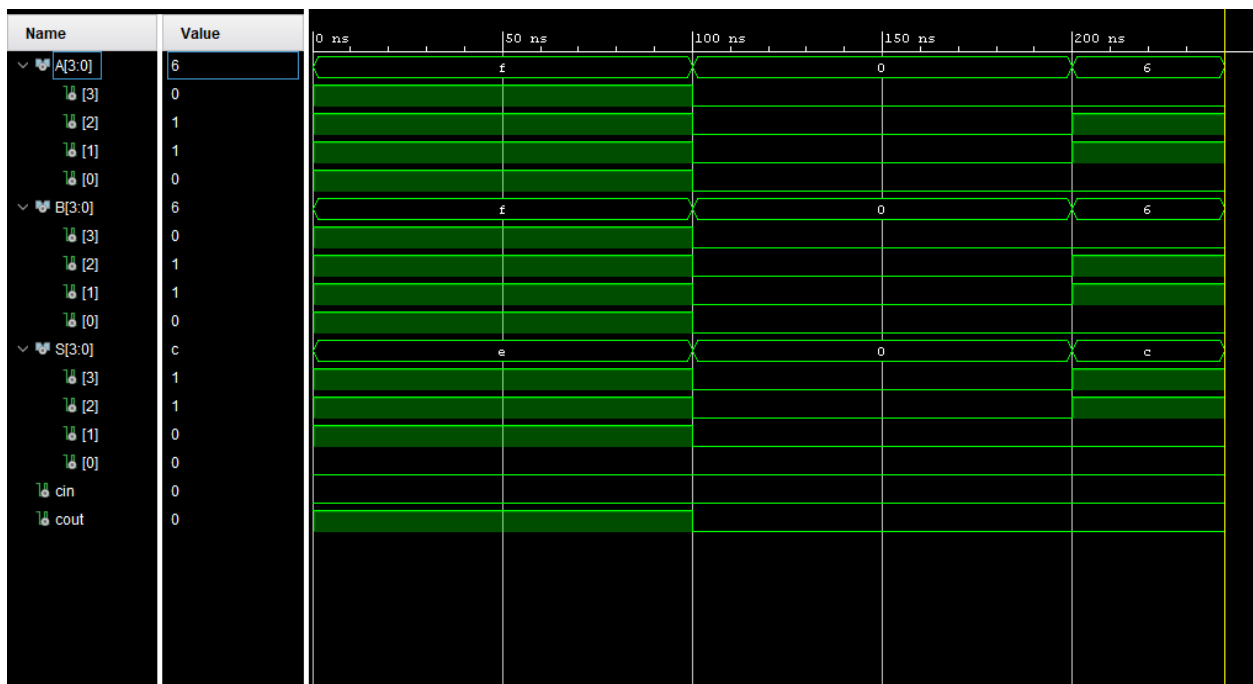

 Same Simulation Window showing only hex values:



SIMULATIONS EXPLAINED:

Three cases were done to test the ripple_counter:

- 1) (A = 1111) + (B=1111) will output S = 1110, cout = 1
 - In this case it will result in overflow, so the correct answer won't be in the output, what will be displayed is 1110 with a carry bit of 1. The cout bit is taking the overflow bit. The cout bit can be thought of as the 5th bit. The output S in the simulation correctly returned "e" which is equal to "1110", with a cout of 1.
- 2) (A = 0000) + (B = 0000) will output S = 0000, cout = 0
 - In the simulation window it shows correctly the output 0 and the carry out bit 0
- 3) (A = 0110) + (B=0110) will output S = 1100, cout = 0
 - In this case the answer should be 12(decimal) = 1100(binary) with a carry out bit, cout = 0.

The simulation correctly output 'c' in hex which is equal to 1100, with a carry outbit, cout = 0.

PART 2

THEORY OF OPERATION:


For this part of the lab, we constructed a 16 function ALU. By taking advantage of the `std_numeric` library, a multi function ALU can be designed without having to code each function independently. We then created a top design that incorporates the 16 function ALU and the debouncer created from a previous lab. The top design called `Alu_tester` will have 3 inputs, **switch** and **button** to two different 4-bit `std_logic_vectors`, and a **clk**. The output will be stored in a 4-bit `std_logic_vector` to **LED**.

The output of the `my_alu` will be connected to **LED**. The values for **A**, **B**, and **OPCODE** from `my_alu` will be assigned to the **SWITCH** inputs. The clock enables for the **OPCODE**, **A**, and **B** registers will be connected to the outputs of the button debouncers. The debouncers are used to stabilize the output of a pressed button. By pressing `button(2)`, and when its Debounced output is high, it will update the **OPCODE** value/register. `Button(1)` updates **A** value, and `Button(0)` updates **B** value. `Button(3)` will reset the signals of **A**, **B**, and **OPCODE** to "0000". Using the button update functionality, we can use one set of 4 switches to update the three signals when desired. All of these operations will only happen on a rising clock edge.


All of this functionality together will enable the use of a 16 function ALU. Assigning values to the **A**, **B**, and **OPCODE** signals are performed by using the buttons and switches. Depending on the opcode, the ALU will perform the corresponding logic/arithmetic operation on **A** and **B** and output the result to the **LED**s.

A demo of this design was performed on a zybo board and with success behaved as expected.


“my_alu” SCHEMATIC:

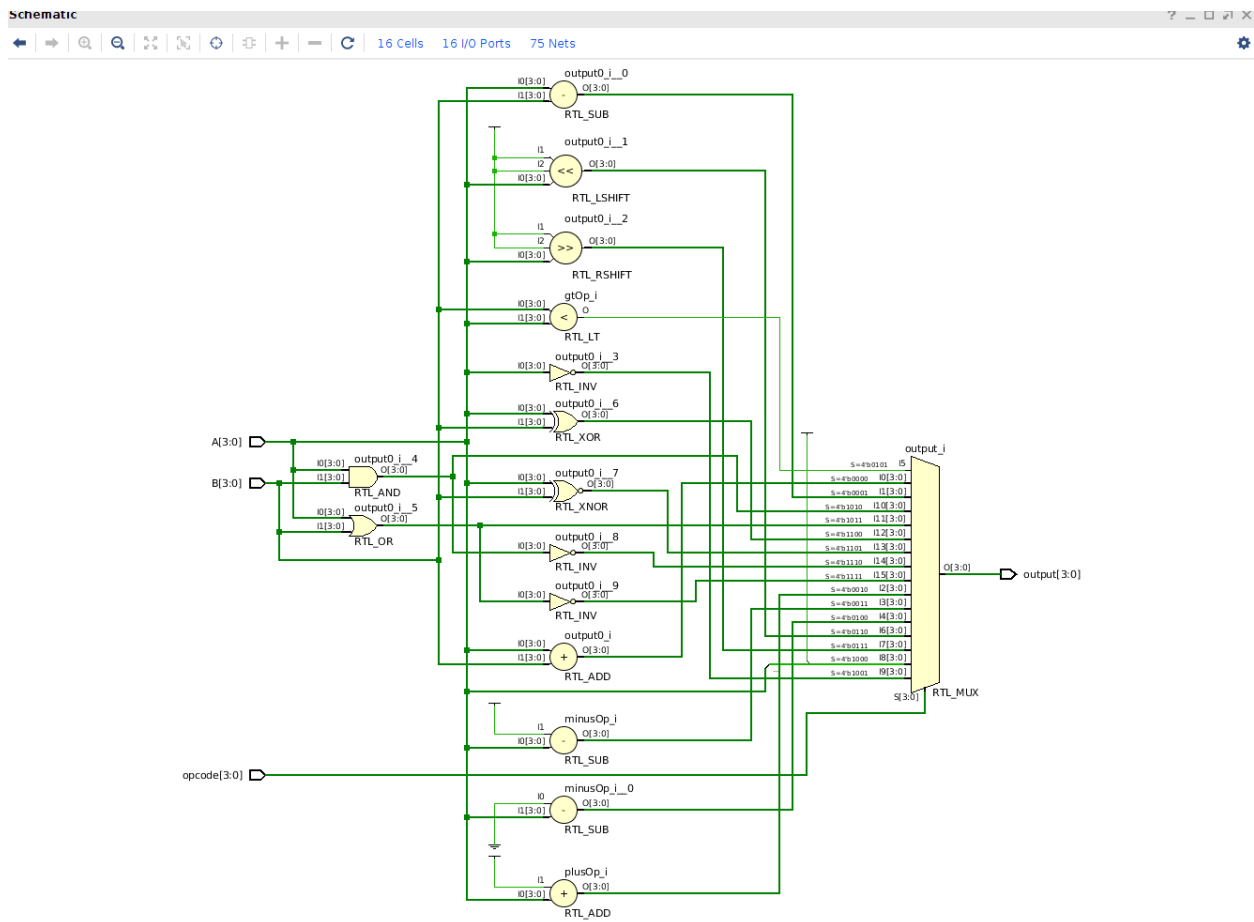

“debounce” SCHEMATIC:

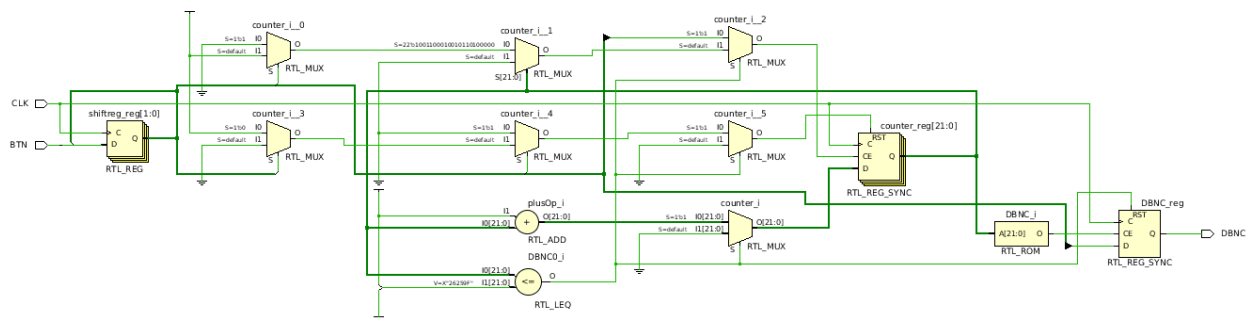

“alu_tester” (top design) SCHEMATIC:

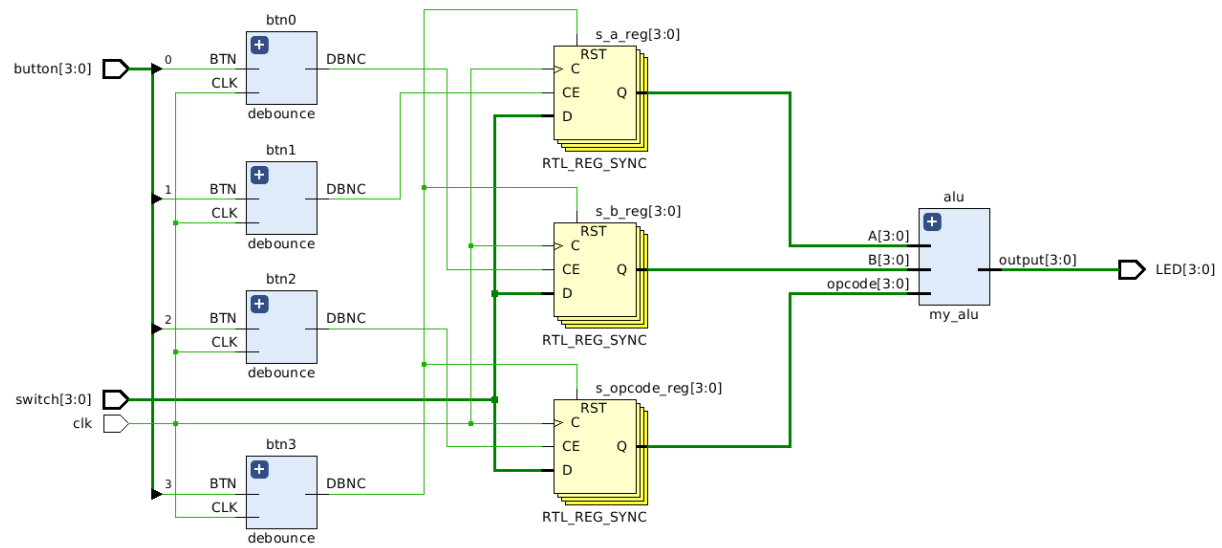

VHDL CODE

my_alu:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;
use IEEE.std_logic_unsigned.all;

entity my_alu is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          opcode : in STD_LOGIC_VECTOR (3 downto 0);
          output : out STD_LOGIC_VECTOR (3 downto 0));
end my_alu;

architecture Behavioral of my_alu is

begin
    process(A,B,opcode)
    begin
        case (opcode) is
            when "0000" => output<= std_logic_vector(unsigned(A) + unsigned(B));
            when "0001" => output<= std_logic_vector(unsigned(A) - unsigned(B));
            when "0010" => output<= std_logic_vector(unsigned(A) + 1);
            when "0011" => output<= std_logic_vector(unsigned(A) - 1);
            when "0100" => output<= std_logic_vector(0- unsigned(A));
            when "0101" => if (A>B) then output<="0001"; else output<= "0000"; end if;
            when "0110" => output<= std_logic_vector(unsigned(A) sll 1);
            when "0111" => output<= std_logic_vector(unsigned(A) srl 1);
            when "1000" => output<= '1' & A(3 downto 1);
            when "1001" => output<= not A;
            when "1010" => output<= A and B;
            when "1011" => output<= A or B;
            when "1100" => output<= A xor B;
            when "1101" => output<= A xnor B;
            when "1110" => output<= A nand B;
            when "1111" => output<= A nor B;
            when others => output<="0000";
        end case;
    end process;

end Behavioral;
```

debounce:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;
```

```
entity debounce is
  Port ( BTN : in STD_LOGIC;
        CLK : in STD_LOGIC;
        DBNC : out STD_LOGIC);
end debounce;
```

```
architecture Behavioral of debounce is
  signal shiftreg : std_logic_vector (1 downto 0) := (others => '0');
  signal counter : std_logic_vector(21 downto 0) := (others => '0');
begin
```

```
  process (clk)
  begin
```

```
    if (rising_edge(clk)) then
      shiftreg(1) <= shiftreg(0);
      shiftreg(0) <= BTN;
```

```
    if (unsigned(counter)<= 2499999) then
      DBNC <= '0';
      if shiftreg(1) = '1' then
        counter <= std_logic_vector(unsigned(counter)+1);
      elsif (shiftreg(1)='0') then
        counter <= (others => '0');
```

```
    end if;
```

```
    elsif (unsigned(counter)= 2500000) then
      if (shiftreg(1)='1') then
        DBNC <='1';
      else
        DBNC <='0';
        counter <= (others => '0');
      end if;
```

```
  end if;
end if;
```

```
end process;
```

```
end Behavioral;
```


alu_tester:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity alu_tester is
  Port ( switch : in STD_LOGIC_VECTOR (3 downto 0);
        button : in STD_LOGIC_VECTOR (3 downto 0);
        clk : in std_logic;
        LED : out STD_LOGIC_VECTOR (3 downto 0));
end alu_tester;
```

architecture Behavioral of alu_tester is

```
component my_alu
port(
A : in STD_LOGIC_VECTOR (3 downto 0);
B : in STD_LOGIC_VECTOR (3 downto 0);
opcode : in STD_LOGIC_VECTOR (3 downto 0);
output : out STD_LOGIC_VECTOR (3 downto 0)
);
end component;
```

```
component debounce
  Port ( BTN : in STD_LOGIC;
        CLK : in STD_LOGIC;
        DBNC : out STD_LOGIC);
end component;
```

```
signal s_dbnc : std_logic_vector(3 downto 0);
signal s_opcode, s_a, s_b : std_logic_vector ( 3 downto 0);
begin
```

```
process(clk)
begin
if (rising_edge(clk)) then
if s_dbnc(3) = '1' then
s_opcode <= "0000";
s_a <= "0000";
s_b <= "0000" ;
else
if s_dbnc(2) = '1' then s_opcode <= switch; end if;
if s_dbnc(1) = '1' then s_a <= switch; end if;
if s_dbnc(0) = '1' then s_b <= switch; end if;
```

```
        end if;  
    end if;  
end process;
```

```
btn3: debounce  
port map(  
    btn => button(3),  
    clk => clk,  
    dbnc => s_dbnc(3)  
);  
btn2: debounce  
port map(  
    btn => button(2),  
    clk => clk,  
    dbnc => s_dbnc(2)  
);  
btn1: debounce  
port map(  
    btn => button(1),  
    clk => clk,  
    dbnc => s_dbnc(1)  
);  
btn0: debounce  
port map(  
    btn => button(0),  
    clk => clk,  
    dbnc => s_dbnc(0)  
);  
alu: my_alu  
port map(  
    A => s_a,  
    B => s_b,  
    opcode => s_opcode,  
    output => LED  
);
```

```
end Behavioral;
```

XDC FILE:

##Clock signal

```
set_property -dict { PACKAGE_PIN L16  IOSTANDARD LVCMOS33 } [get_ports  
{ clk }]; #IO_L11P_T1_SRCC_35 Sch=sysclk  
create_clock -add -name sys_clk_pin -period 8.00 -waveform {0 4} [get_ports  
{ clk }];
```


##Switches

```
set_property -dict { PACKAGE_PIN G15  IOSTANDARD LVCMOS33 } [get_ports  
{ switch[0] }]; #IO_L19N_T3_VREF_35 Sch=SW0  
set_property -dict { PACKAGE_PIN P15  IOSTANDARD LVCMOS33 } [get_ports  
{ switch[1] }]; #IO_L24P_T3_34 Sch=SW1  
set_property -dict { PACKAGE_PIN W13  IOSTANDARD LVCMOS33 } [get_ports  
{ switch[2] }]; #IO_L4N_T0_34 Sch=SW2  
set_property -dict { PACKAGE_PIN T16  IOSTANDARD LVCMOS33 } [get_ports  
{ switch[3] }]; #IO_L9P_T1_DQS_34 Sch=SW3
```


##LEDs

```
set_property -dict { PACKAGE_PIN M14  IOSTANDARD LVCMOS33 } [get_ports  
{ LED[0] }]; #IO_L23P_T3_35 Sch=LED0  
set_property -dict { PACKAGE_PIN M15  IOSTANDARD LVCMOS33 } [get_ports  
{ LED[1] }]; #IO_L23N_T3_35 Sch=LED1  
set_property -dict { PACKAGE_PIN G14  IOSTANDARD LVCMOS33 } [get_ports  
{ LED[2] }]; #IO_0_35=Sch=LED2  
set_property -dict { PACKAGE_PIN D18  IOSTANDARD LVCMOS33 } [get_ports  
{ LED[3] }]; #IO_L3N_T0_DQS_AD1N_35 Sch=LED3  
set_property -dict { PACKAGE_PIN R18  IOSTANDARD LVCMOS33 } [get_ports  
{ button[0] }]; #IO_L23P_T3_35 Sch=LED0  
set_property -dict { PACKAGE_PIN P16  IOSTANDARD LVCMOS33 } [get_ports  
{ button[1] }]; #IO_L23N_T3_35 Sch=LED1  
set_property -dict { PACKAGE_PIN V16  IOSTANDARD LVCMOS33 } [get_ports  
{ button[2] }]; #IO_0_35=Sch=LED2  
set_property -dict { PACKAGE_PIN Y16  IOSTANDARD LVCMOS33 } [get_ports  
{ button[3] }]; #IO_L3N_T0_DQS_AD1N_35 Sch=LED3
```

ELABORATION SCHEMATIC:

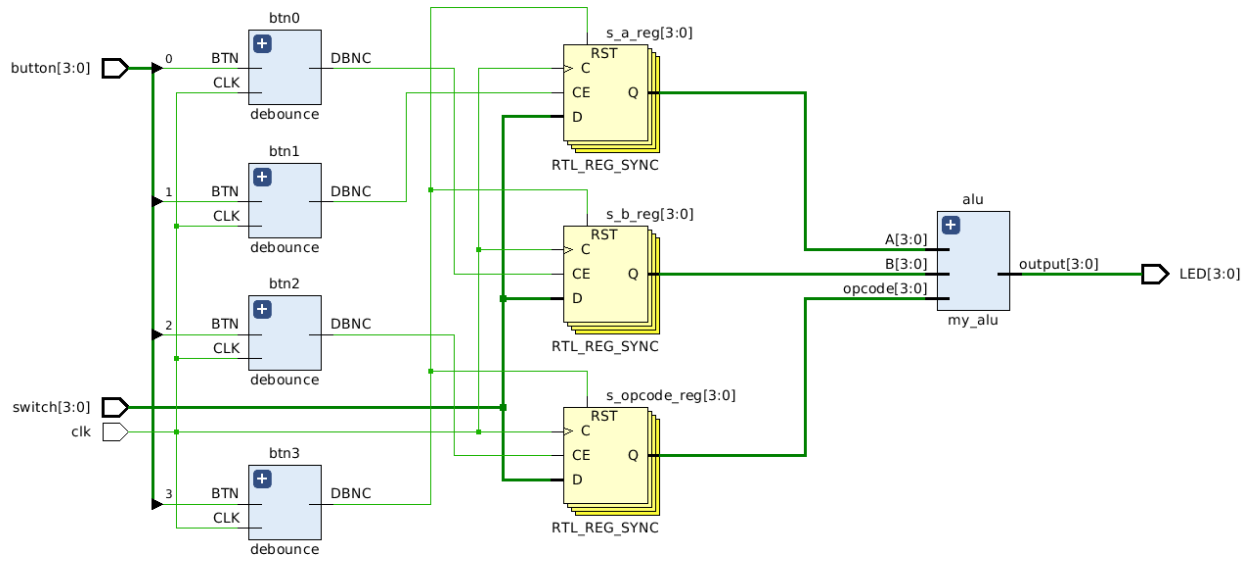


SYNTHESIS SCHEMATIC:

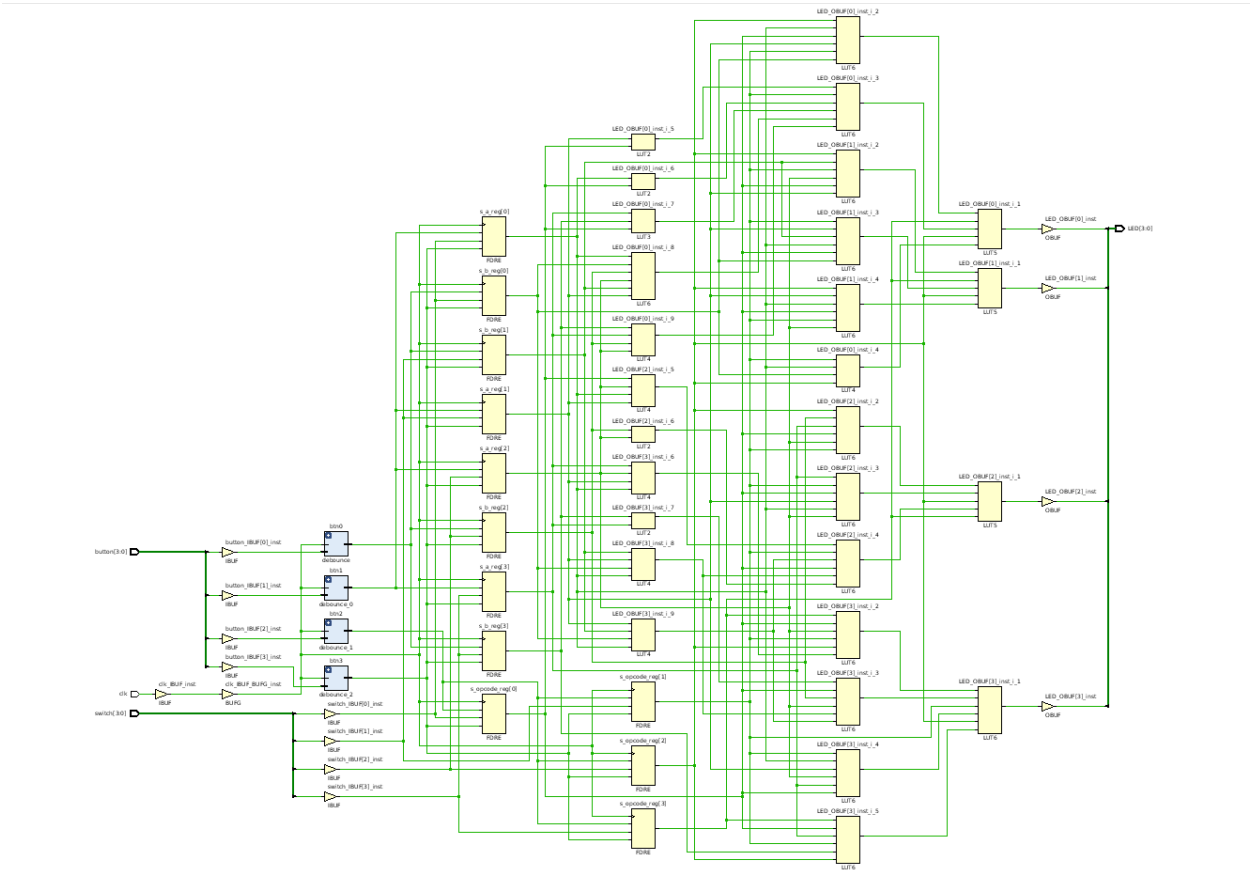

UTILIZATION:

Summary

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT | 171 | 17600 | 0.97 |
| FF | 112 | 35200 | 0.32 |
| IO | 13 | 100 | 13.00 |

 

POWER:


Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.


Total On-Chip Power: 0.091 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.1°C
Thermal Margin: 58.9°C (5.0 W)
Effective θ_{JA} : 11.5°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity


On-Chip Power

 

DEVICE:

 

DEVICE ZOOMED IN:

 

XDC FILE CHANGES:

The clk input is connected to pin L16 (125 mHz clock).

The switch input bits 0-4 are connected respectively to pin G15, P15, W13, T16.

The LED output bits are connected respectively to the boards led pins M14, M15, G14, D18.

The 4 button inputs are respectively connected to pins R18, P16, V16, Y16.

These inputs and outputs cover all the I/O for this design.

DISCUSSION:

It was interesting how the buttons were used to update the OPCODE, A, and B signals. It enabled us to not need three sets of switches to update each signal. By using the buttons we only needed one set of switches. Seeing this implementation made me think of reduction in components and therefore save money on design.